

# Ohm's Law

Relation between  $V$ ,  $I$  &  $R$  (Ohm's law)

All the electrical Elements are satisfy this Ohm's law

Use of Ohm's law  $\rightarrow$  provide the relation between  $V$ ,  $I$ , &  $R$ .

Statement:

At Constant temperature, the ratio between potential difference ( $V$ ), across the two ends of the conductor and current through it, is constant.

$$R = \frac{V}{I}$$

@ Constant temperature.

Other forms of law,

$$R = \frac{V}{I} \quad \text{or} \quad I = \frac{V}{R} \quad \text{or} \quad V = IR$$

@ Constant temperature

# Kirchoff's Law

1) Kirchoff's current law (KCL)

2) Kirchoff's voltage law (KVL)

KCL [ Kirchoff's current Law ]

→ Mesh current law

(K) Current cannot be stored at any point in a circuit

Current → Move (or) flow of charges.

Entering current (or) incoming current (+) = }  $\frac{V}{R} = I$  leaving current (or) outgoing current (-)

$$\sum \text{of incoming current} + \sum \text{of outgoing current} = 0$$


\* The Amount of current entering to a point must leave the point.

Statement:


The Algebraic Sum of the currents meeting at a point is equal to zero.

$$\sum I = 0 \Rightarrow \sum I_{EC} = \sum I_{LC}$$

$$\sum I_{EC} + \sum I_{LC} = 0$$

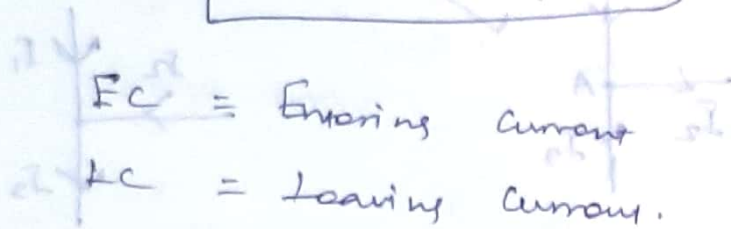

Explanation:

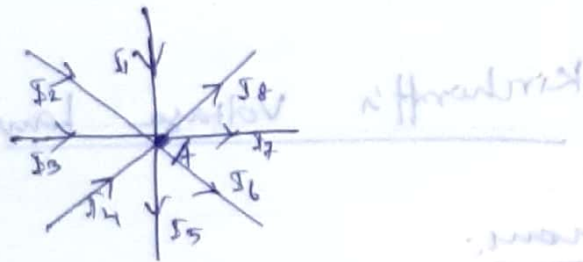

$I_1, I_2, I_3, I_4$  = Entering current.

$I_5, I_6, I_7, I_8$  = Leaving current.

$$I_1 + I_2 + I_3 + I_4 = I_5 + I_6 + I_7 + I_8$$

$$I_1 + I_2 + I_3 + I_4 - (I_5 + I_6 + I_7 + I_8) = 0$$





$$\sum I_{EC} - \sum I_{LC} = 0$$

$$\sum I_{EC} + \sum I_{LC} = 0$$



Condition:

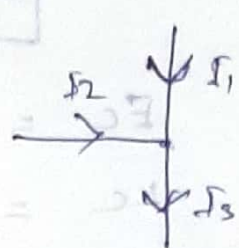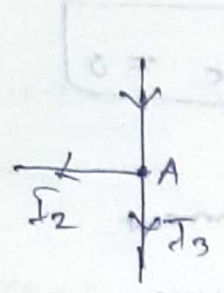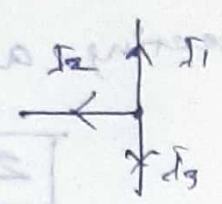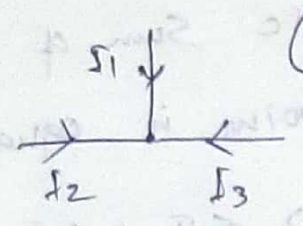\* at least one path must be incoming current and at least one path must be leaving current.



Kirchhoff's Voltage Law.




Statement:

In a closed circuit, the Algebraic Sum of product of current(s) and Resistance (R) ( $\sum IR$ ) + Algebraic sum of Voltage ( $\sum V$ ) is equal to Zero.


$$\sum IR + \sum V = 0$$
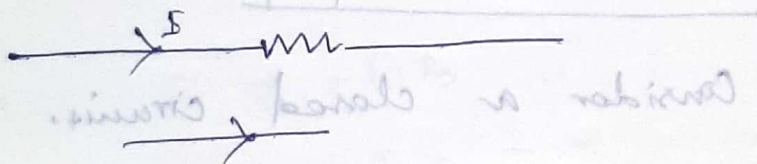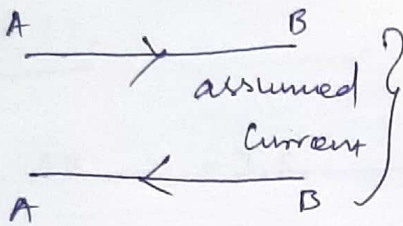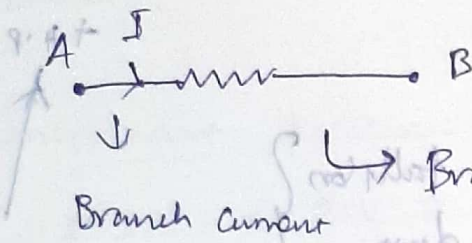
# Sign of IR

The Electric path between two points is called branch → current passing through branch is called branch current.



$IR \rightarrow$  positive sign (+)

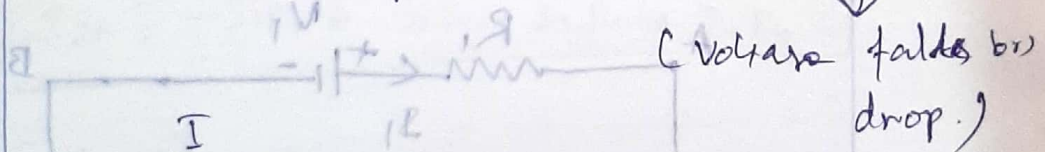

$IR \rightarrow$  Negative sign (-)





∴ IR sign is based on the assumed current.



Sign of  $V$

Sign of IR

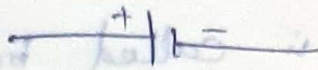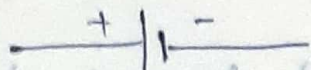

Assumed current


Current

$+V$   
 $+V$  (H.P)

$-V$  (L.P) { Voltage falls (or) " drop.

$+H.P$


$-L.C$

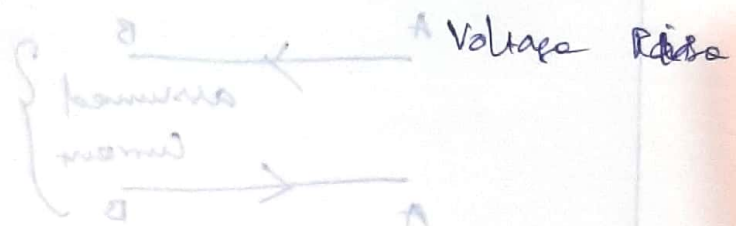

Explanation (or) proof:

Consider a closed circuit.

→ ABCDA.

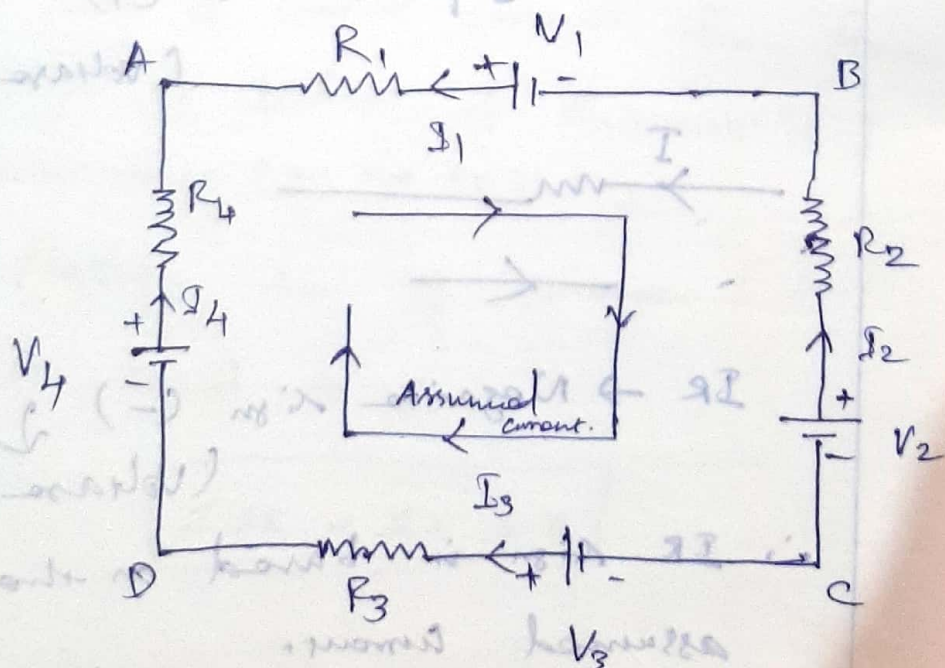

Branches  $\rightarrow$  AB, BC, CD, DA.

$I_1, I_2, I_3, I_4 \rightarrow$  Branch current due to  
 $\downarrow$   $V_1, V_2, V_3 \text{ \& } V_4.$

Directions of the current from positive of Battery.

\* Important parameter of KVL are

$$\sum IR \text{ \& } \sum V$$

Find  $\sum IR$

Branch AB  $\rightarrow -I_1 R_1 \rightarrow$  Voltage Rise

" BC  $\rightarrow -I_2 R_2 \rightarrow$  Voltage "

" CD  $\rightarrow +I_3 R_3 \rightarrow$  " drop

" DA  $\rightarrow +I_4 R_4 \rightarrow$  " "

$$\sum IR = -I_1 R_1 - I_2 R_2 + I_3 R_3 + I_4 R_4$$

Find  $\sum V$

Branch AB  $\rightarrow +V_1 \rightarrow$  voltage drop  
 " BC  $\rightarrow +V_2 \rightarrow$  " "  
 " CD  $\rightarrow -V_3 \rightarrow$  " Rise  
 " DA  $\rightarrow -V_4 \rightarrow$  " "



$$\sum V = V_1 + V_2 - V_3 - V_4$$

KVL,

$$\sum IR + \sum V = 0$$

$$-I_1 R_1 - I_2 R_2 + I_3 R_3 + I_4 R_4 + V_1 + V_2 - V_3 - V_4 = 0$$


$$I_3 R_3 + I_4 R_4 + V_1 + V_2 = I_1 R_1 + I_2 R_2 + V_3 + V_4$$

Sum of Voltage drop = Sum of Voltage Rise


$$\sum V \cdot D = \sum V \cdot R$$

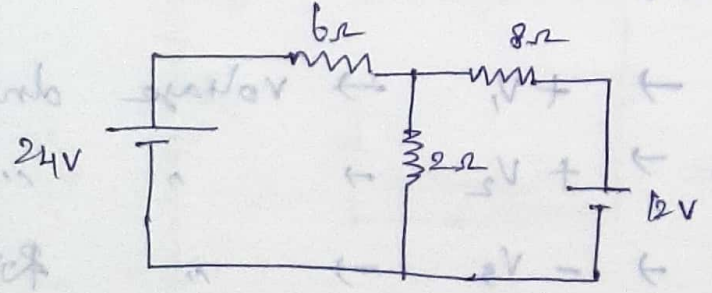Problem No: 1

By using Kirchoff's law, find the current supplied by the Battery, and the current through 2Ω Resistor for the given Circuit.





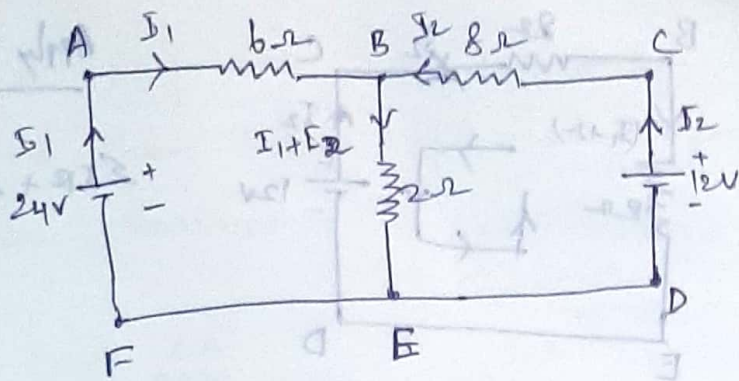


At point B  $\Rightarrow I_1 + I_2 = I_3$

To find  $I_1$  &  $I_2$  we need two equations.

Divide the circuit in two.

- 1) AB EFA
- 2) BCDEB
- 3) ABCDEFA

Closed cir

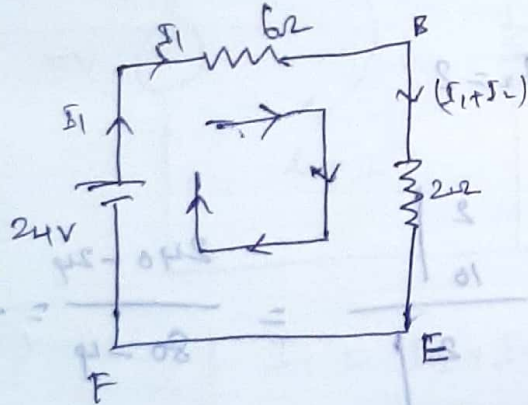

Apply KVL,


$$\sum IR + \sum V = 0$$

$$6I_1 + 2(I_1 + I_2) + (-24) = 0$$

$$6I_1 + 2I_1 + 2I_2 = 24$$

$$8I_1 + 2I_2 = 24 \rightarrow \textcircled{1}$$

closed loop BCDEB

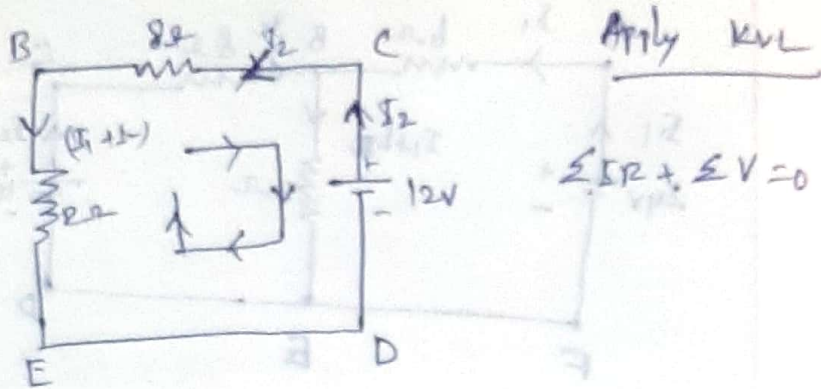

$$-8I_2 + [2(I_1 + I_2)] + 12V = 0$$

$$-8I_2 - 2I_1 - 2I_2 + 12V = 0$$

$$-2I_1 - 10I_2 = -12V$$

$$2I_1 + 10I_2 = 12 \quad \text{--- (2)}$$

$$8I_1 + 2I_2 = 24$$

$$2I_1 + 10I_2 = 12$$

$$I_1 = 2$$

$$I_2 = 2$$

$$I_1 = \frac{\begin{vmatrix} 24 & 2 \\ 12 & 10 \end{vmatrix}}{\begin{vmatrix} 8 & 2 \\ 2 & 10 \end{vmatrix}} = \frac{240 - 24}{80 - 4} = \frac{216}{76} = 2.842 \text{ A}$$

$$I_1 = 2.842 \text{ A}$$

$$I_2 = \frac{\begin{vmatrix} 8 & 24 \\ 2 & 12 \end{vmatrix}}{\begin{vmatrix} 8 & 2 \\ 2 & 10 \end{vmatrix}} = \frac{96 - 48}{80 - 4} = \frac{48}{76} = 0.631 \text{ A}$$

$$I_1 + I_2 = 3.473 \text{ A}$$


$$I_2 = 0.631 \text{ A}$$

$$I_1 + I_2 = 3.473 \text{ A}$$



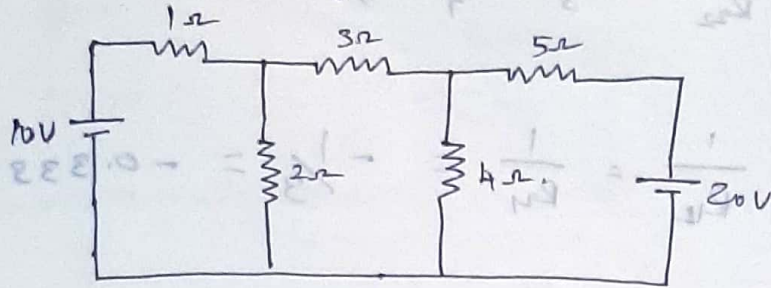
# Nodal Analysis.

① Find the current through each resistor using nodal analysis method.



Solution:

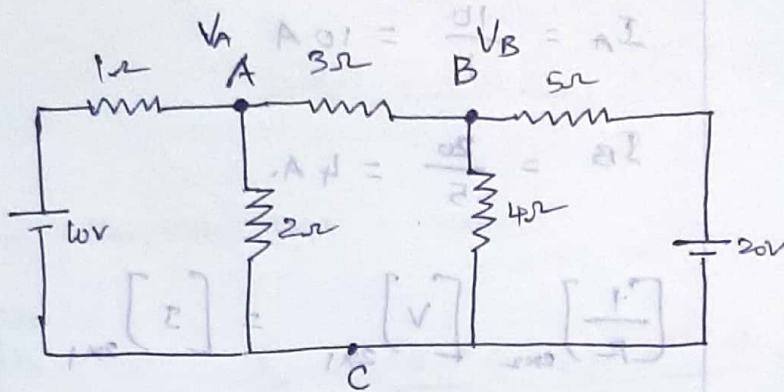

$$V_C = 0$$

Number of Nodes = 3 = N.

$$\left[ \frac{1}{R} \right]_{(N-1) \times (N-1)} [V]_{(N-1) \times 1} = I_{(N-1) \times 1}$$


$$\left[ \frac{1}{R} \right]_{2 \times 2} = \begin{bmatrix} \frac{1}{R_{11}} & \frac{1}{R_{12}} \\ \frac{1}{R_{21}} & \frac{1}{R_{22}} \end{bmatrix}$$

$$[V]_{2 \times 1} = \begin{bmatrix} V_A \\ V_B \end{bmatrix}; [I]_{2 \times 1} = \begin{bmatrix} I_A \\ I_B \end{bmatrix}$$

$$A_{2 \times 2} = \frac{81 \mu \cdot J - 0 \cdot 0}{1} = \frac{1V - 0V}{1}$$

$$\frac{1}{R_1} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} = 1 + 0.5 + 0.333 = 1.833$$
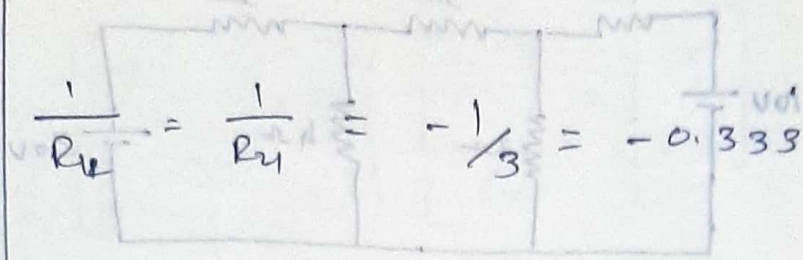
$$\frac{1}{R_2} = \frac{1}{3} + \frac{1}{4} + \frac{1}{5} = 0.333 + 0.25 + 0.2 = 0.783$$



$$\frac{1}{R_1} = \frac{1}{R_2} = -\frac{1}{3} = -0.333$$

$$I_A = \frac{10}{1} = 10 \text{ A}$$

$$I_B = \frac{20}{5} = 4 \text{ A}$$

$$\begin{bmatrix} \frac{1}{R} \end{bmatrix}_{2 \times 2} \begin{bmatrix} V \end{bmatrix}_{2 \times 1} = \begin{bmatrix} I \end{bmatrix}_{2 \times 1}$$

$$\begin{bmatrix} 1.833 & -0.333 \\ -0.333 & 0.783 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 10 \\ 4 \end{bmatrix}$$

Apply Cramer's rule

$$V_A = 6.918 \text{ V}$$

$$V_B = 8.05 \text{ V}$$

Current through  $1 \Omega$

$$I_1 = \frac{10 - V_A}{1} = \frac{10 - 6.918}{1} = 3.08 \text{ A}$$




Current through  $2\Omega$



$$I_2 = \frac{V_A - V_C}{2} = \frac{6.918}{2} = 3.459 \text{ A}$$

Current through  $3\Omega$

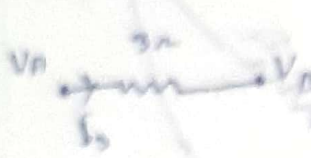

$$I_3 = \frac{V_A - V_B}{3} = \frac{6.918 - 8.05}{3}$$

$$I_3 = -0.37 \text{ A}$$

$$I_3 = -0.37 \text{ A}$$


Current through  $4\Omega$



$$I_4 = \frac{V_B - V_C}{4} = \frac{8.05 - 0}{4} = 2.0125 \text{ A}$$

$$I_4 = 2.0125 \text{ A}$$

Current through  $5\Omega$

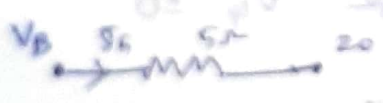


$$I_5 = \frac{V_B - 20}{5} = \frac{8.05 - 20}{5} = -2.39 \text{ A}$$

$$\begin{bmatrix} 1 \\ -1 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ -2 \\ 0 \end{bmatrix} \cdot \begin{bmatrix} \frac{1}{1\Omega} & \frac{1}{2\Omega} & \frac{1}{5\Omega} \\ \frac{1}{2\Omega} & \frac{1}{3\Omega} & \frac{1}{4\Omega} \\ \frac{1}{5\Omega} & \frac{1}{4\Omega} & \frac{1}{2\Omega} \end{bmatrix}$$

# Voltage & current division Rule

## Voltage division Rule

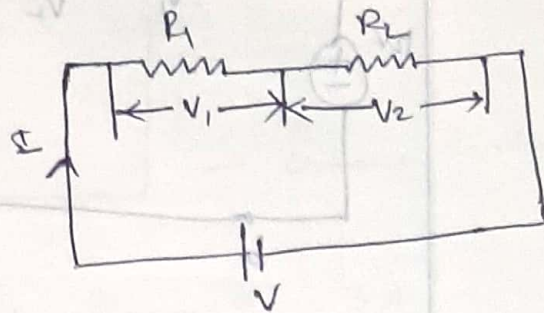


$$V_1 = \frac{\text{Total voltage} \times \text{Corresponding Resistance}}{\text{Sum of the resistances}}$$

$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

## Current division Rule

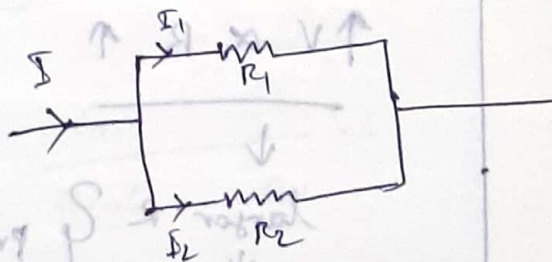


$$I_1 = \frac{\text{Total current} \times \text{Opposite Resistance}}{\text{Sum of the resistances}}$$

$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$\therefore I_2 = \frac{I \times R_1}{R_1 + R_2}$$



# Series Resistor & Voltage Division:

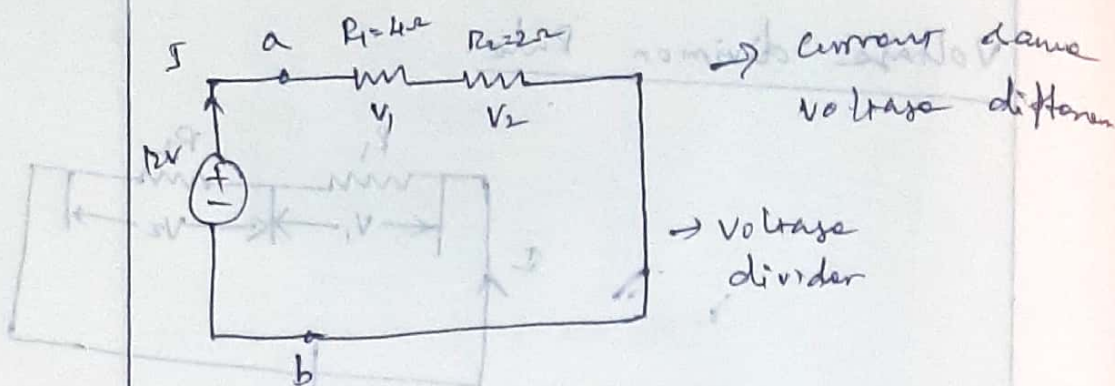


$$V_1 = \frac{R_1}{R_1 + R_2} \times V = \frac{4}{4 + 2} \times 12 = 8V$$

$$V_2 = \frac{R_2}{R_1 + R_2} \times V = \frac{2}{4 + 2} \times 12 = 4V$$

For n-Resistor:

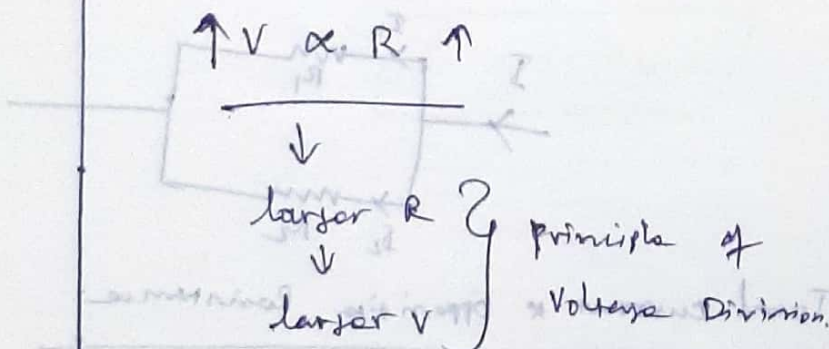
$$V_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} \times V$$



$$\frac{R_1}{R_1 + R_2} = \dots$$

$$\frac{R_2}{R_1 + R_2} = \dots$$

# Parallel Resistors & Current Division

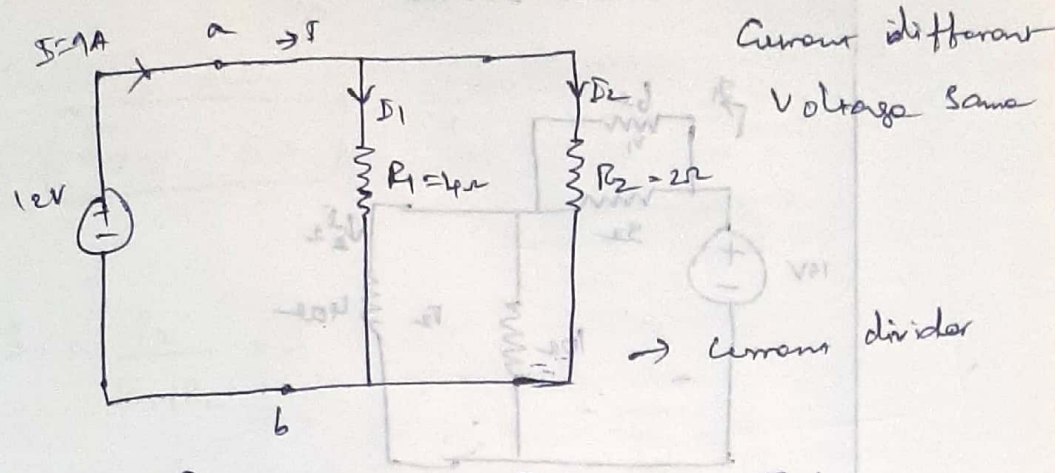

$$I_1 = \frac{R_2}{R_1 + R_2} \times I = \frac{2}{4 + 2} \times 9 = 3A$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times I = \frac{4}{4 + 2} \times 9 = 6A$$

$$R_{eqn} = \frac{R_1 R_2}{R_1 + R_2} = \frac{4 \times 2}{4 + 2} = \frac{8}{6} = 1.332\Omega$$

$$V = IR \Rightarrow I = \frac{V}{R} = \frac{12}{1.333} = 9A$$

$$I = \frac{Q}{t}, \quad V = \frac{J}{Q}$$

$$\frac{1}{R} = G$$

$$I_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} \times I$$

$$\downarrow I \propto \frac{1}{R \uparrow}$$


larger R  
↓  
smaller I

Principle of Current division




# Source Transformation

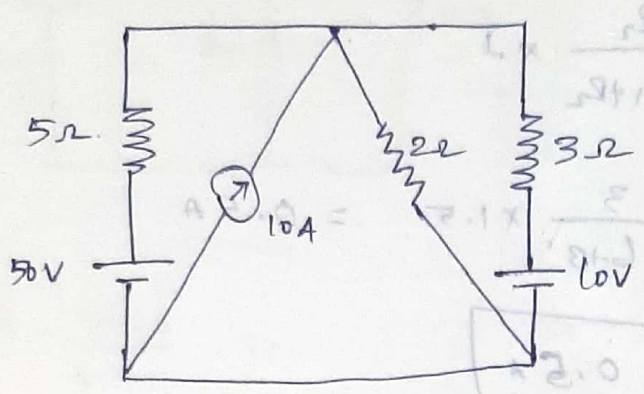1) Using source transformation, find the power delivered by the 50V voltage source.



Solution:

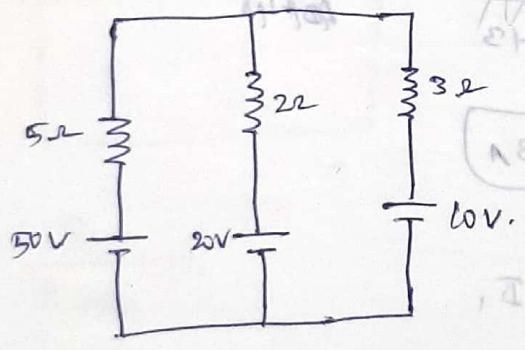→ Convert the current source into voltage source.




$$V = IR$$

$$= 10 \times 2$$

$$= 20V$$

⇓

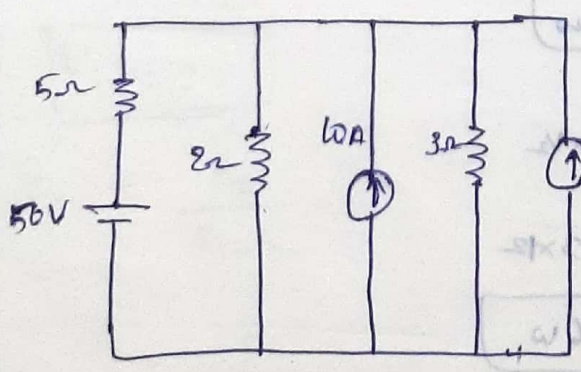


$$I = \frac{V}{R}$$

$$= \frac{20}{2} = 10A$$


$$I = \frac{10}{3} = 3.33$$

⇓

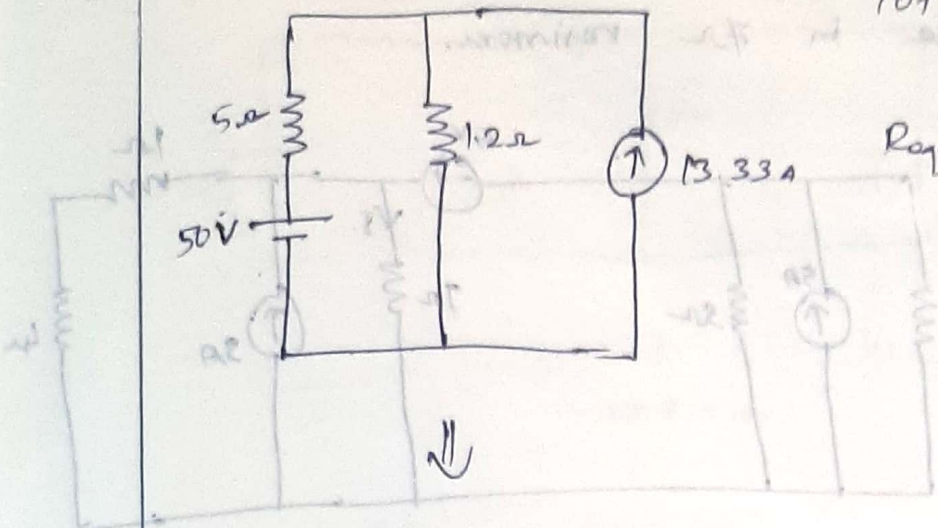

$$10 + 3.33A = 13.33A$$
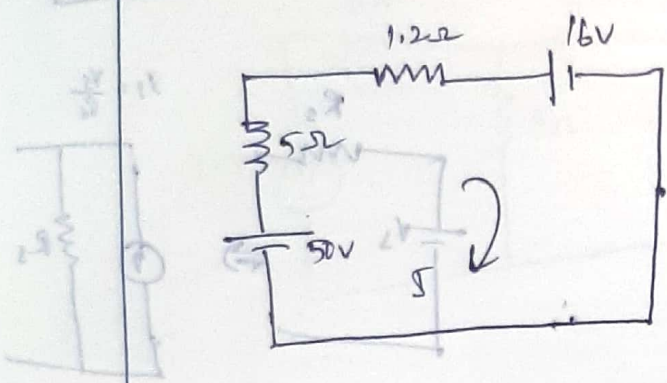
$$R_{eq} = \frac{10 \times 3}{10 + 3} = 1.2\Omega$$




$$V = IR$$

$$= 13.33 \times 1.2$$

$$= 16V$$

Apply KVL to the loop.

$$50 - 5I - 1.2I - 16 = 0$$

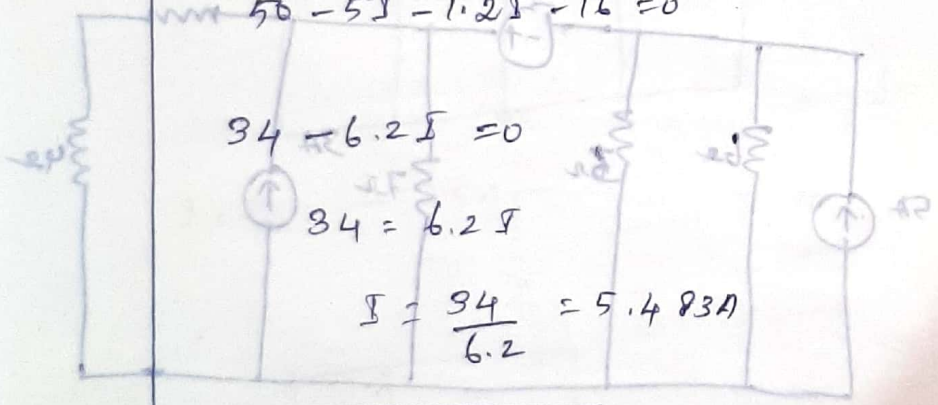

$$34 - 6.2I = 0$$

$$34 = 6.2I$$

$$I = \frac{34}{6.2} = 5.483A$$

$$I = 5.483A$$


Power delivered by the 50V source =  $V \cdot I$

$$= 50 \times 5.483$$




$$P = 274.19W$$



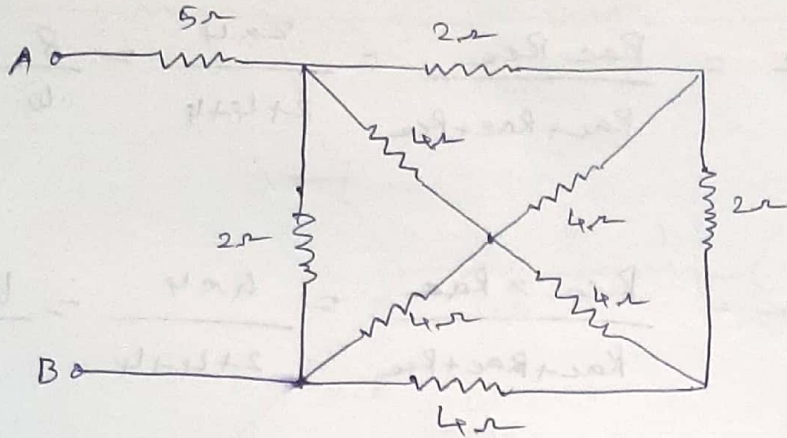② Use delta - star conversion, find resistance between terminal A & B.




Solution.

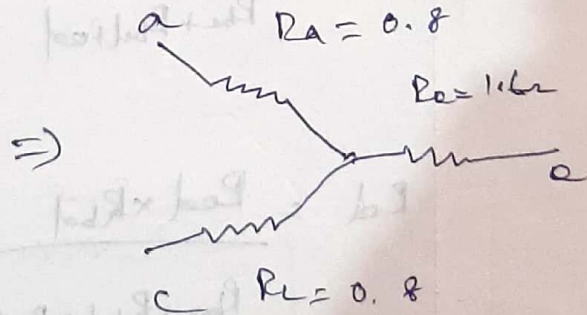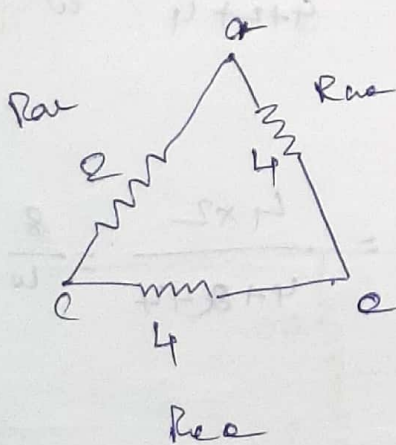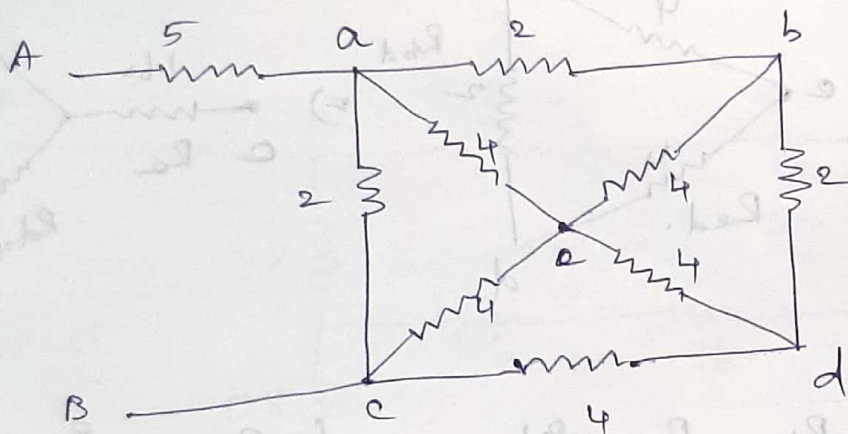

$$R_a = \frac{R_{ac} \times R_{ce}}{R_{ac} + R_{ce} + R_{ca}} = \frac{2 \times 4}{2 + 4 + 4} = \frac{8}{10} = 0.8 \Omega$$

$$R_c = \frac{R_{ac} R_{ce}}{R_{ac} + R_{ce} + R_{ca}} = \frac{2 \times 4}{2 + 4 + 4} = \frac{8}{10} = 0.8 \Omega$$
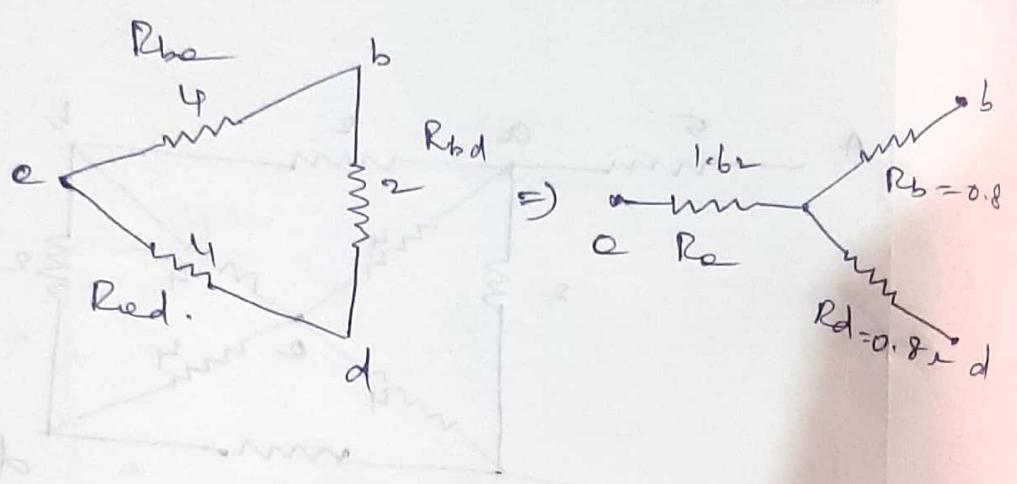
$$R_e = \frac{R_{ce} \times R_{ca}}{R_{ac} + R_{ce} + R_{ca}} = \frac{4 \times 4}{2 + 4 + 4} = \frac{16}{10} = 1.6 \Omega$$




$$R_b = \frac{R_{be} \times R_{bd}}{R_{be} + R_{bd} + R_{ed}} = \frac{4 \times 2}{4 + 2 + 4} = \frac{8}{10} = 0.8 \Omega$$



$$R_d = \frac{R_{ed} \times R_{bd}}{R_{be} + R_{bd} + R_{ed}} = \frac{4 \times 2}{4 + 2 + 4} = \frac{8}{10} = 0.8 \Omega$$


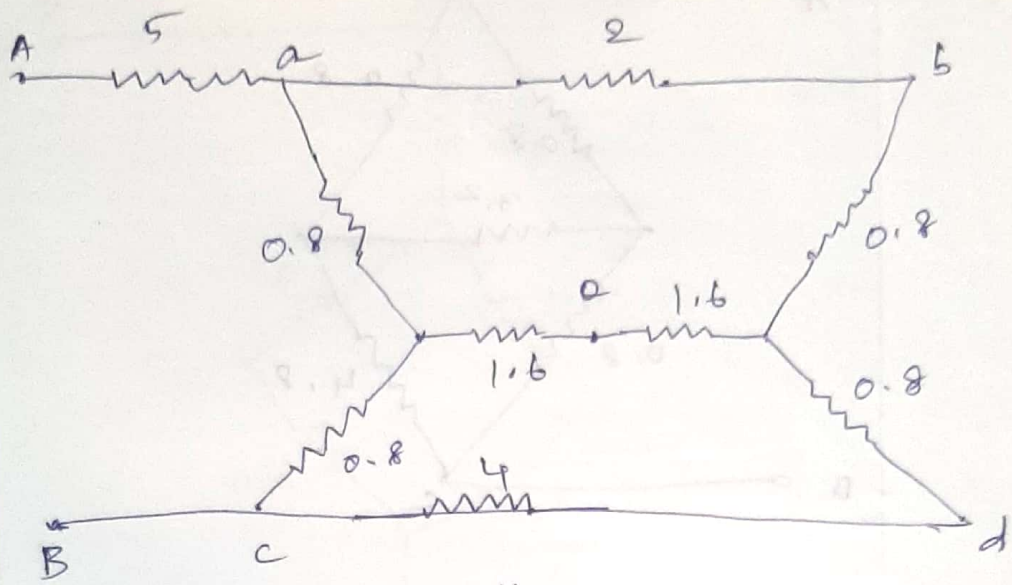
$$R_e = \frac{R_{ed} \times R_{be}}{R_{be} + R_{bd} + R_{ed}} = \frac{4 \times 4}{4 + 2 + 4} = \frac{16}{10} = 1.6 \Omega$$





||

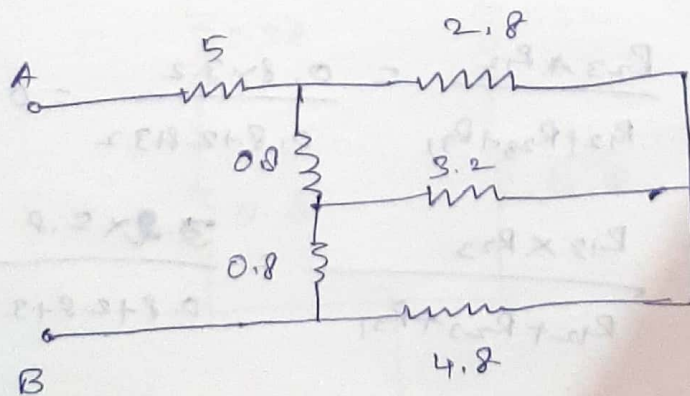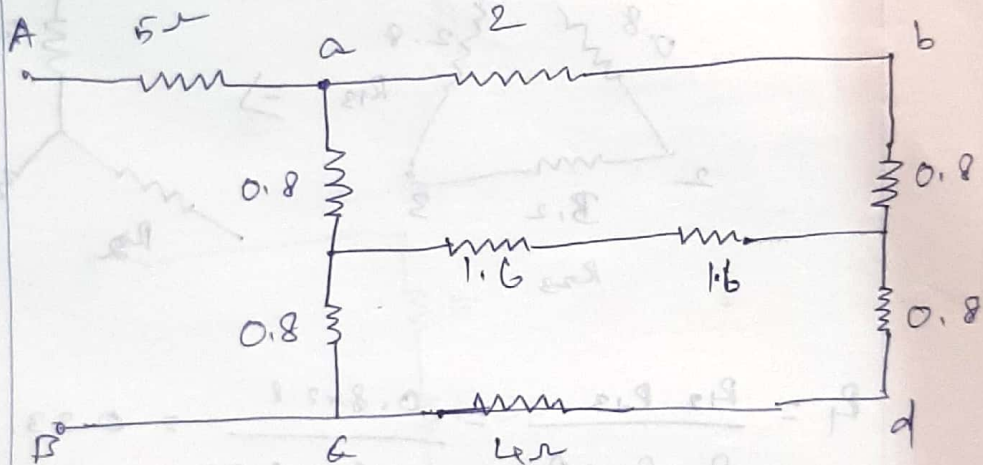

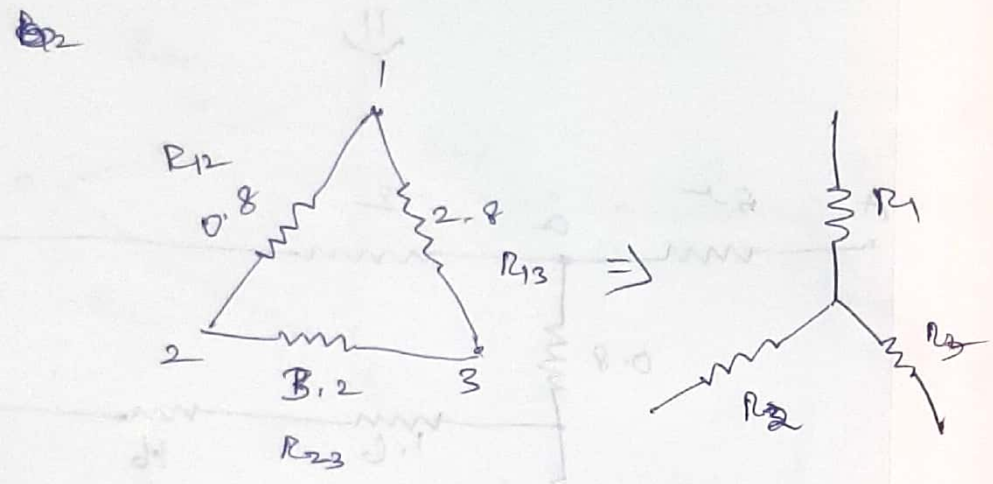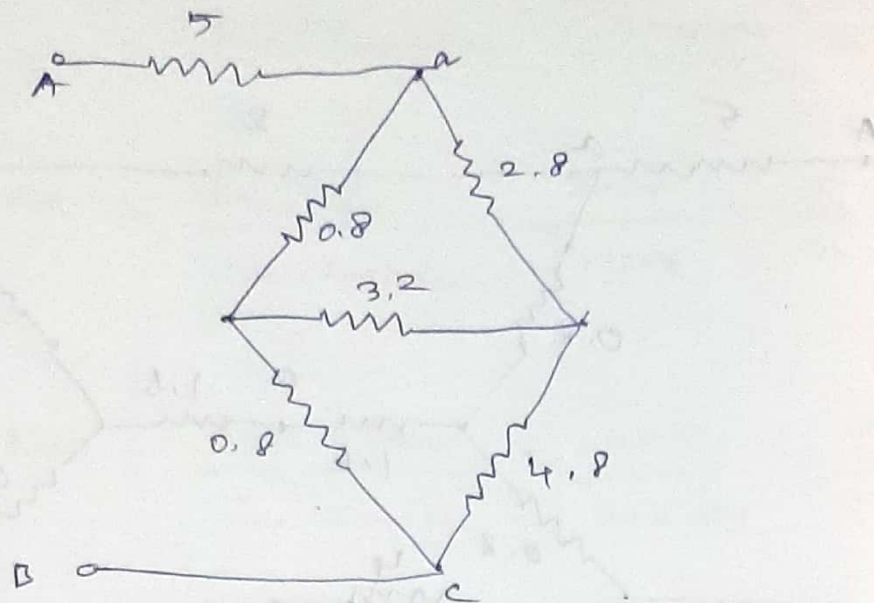


$$R_1 = \frac{R_{12} R_{13}}{R_{12} + R_{23} + R_{31}} = \frac{0.8 \times 2.8}{0.8 + 2.8 + 3.2} = 0.33$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{0.8 \times 3.2}{0.8 + 2.8 + 3.2} = 0.38$$

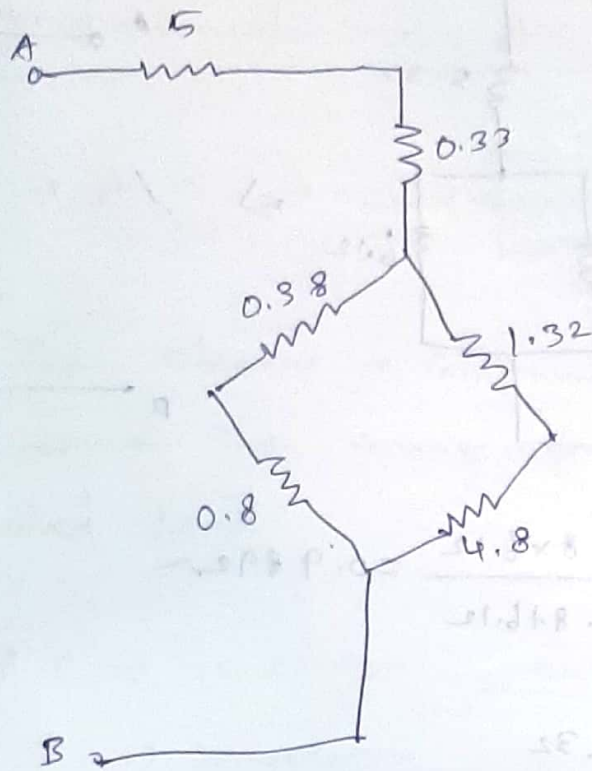
$$R_3 = \frac{R_{13} \times R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{3.2 \times 2.8}{0.8 + 2.8 + 3.2} = 1.32$$







↓

$R_{AB} = 6.33 \Omega$

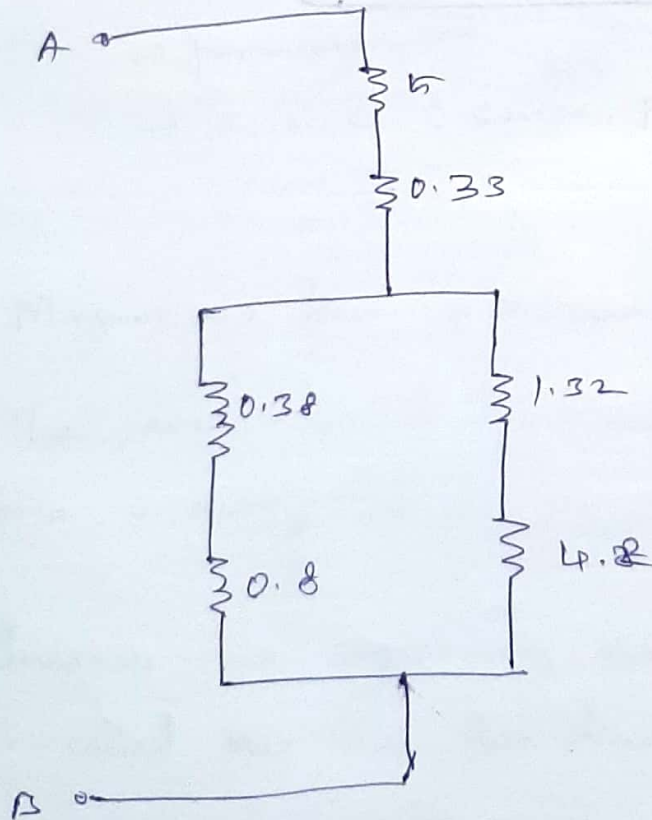

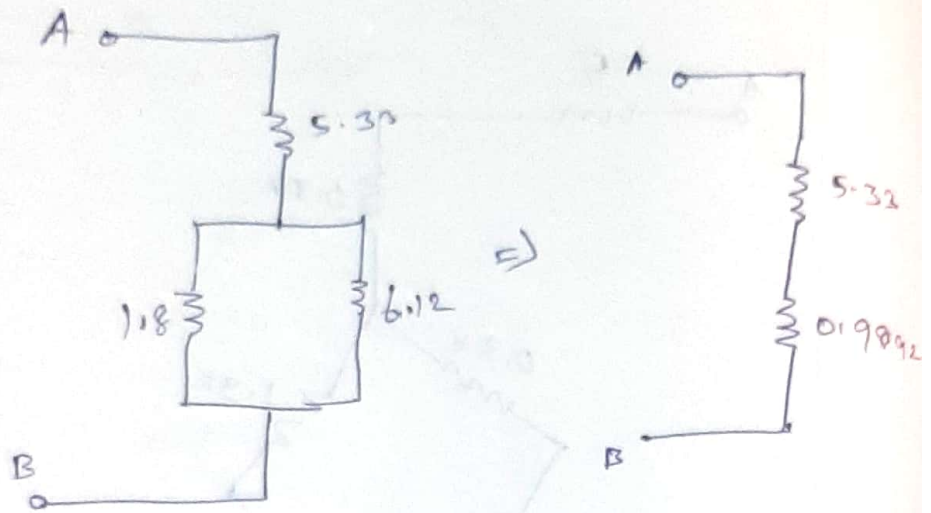

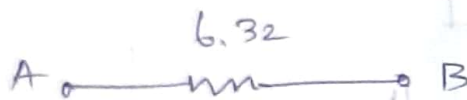
$$R = \frac{1.8 \times 6.12}{1.8 + 6.12} = 0.9892 \Omega$$



$$R_{AB} = 6.32 \Omega$$



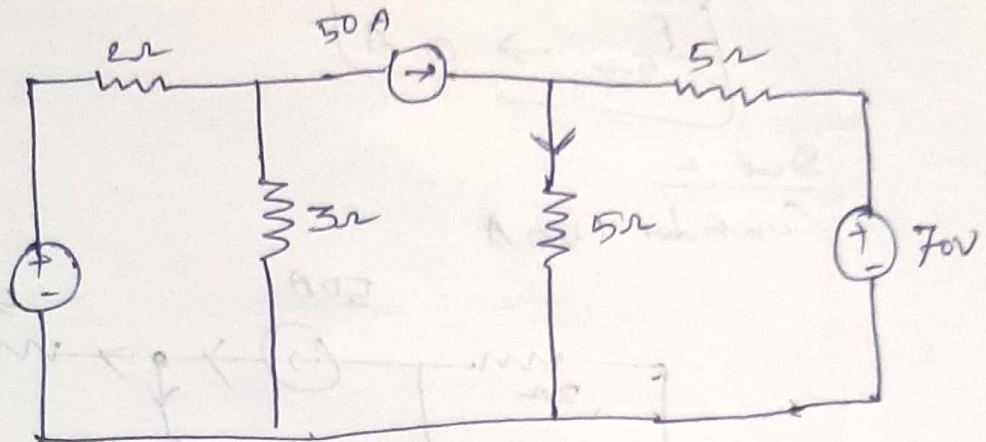② Find current through  $5\Omega$  using Superposition theorem.



Solution.

→ Consider one source at a time

→ Neglect remaining sources.

→ while neglecting,

make Voltage source  $\rightarrow$  S.C

Current "  $\rightarrow$  O.C

Making the value of voltage & current source Zero

In S.C

$$R \rightarrow 0, I \rightarrow \infty$$

$$V = IR \quad V \rightarrow 0$$

$$I = \frac{V}{R}$$


In O.C

$$R \rightarrow \infty$$

$$I \rightarrow 0$$


$$V \rightarrow \infty$$

Step: 1 Consider 100V

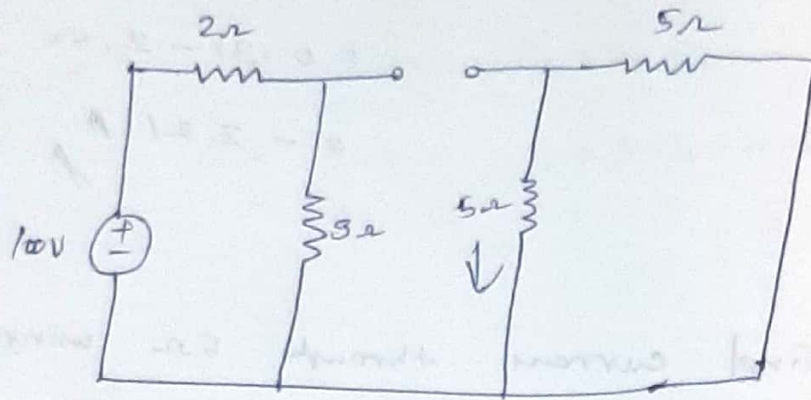

$$I_{5\Omega} \rightarrow 0A$$


Step: 2  
Consider 50A

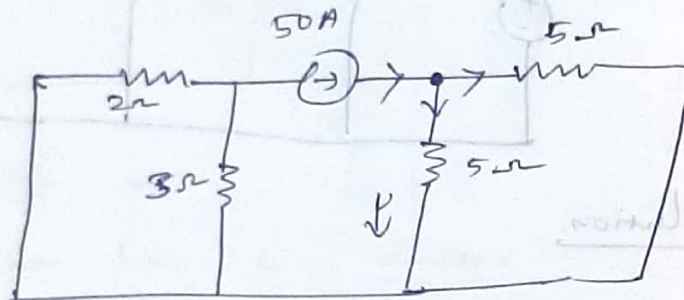

$$I_{5\Omega}'' = 25A$$

Step: 3

Consider 70V

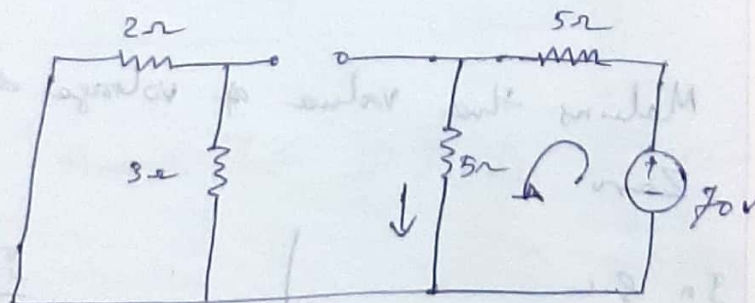

$$5 + 5 = 10\Omega$$

$$I = \frac{70}{10} = 7A$$

$$I_{5\Omega}''' = 7A$$




Step: 3

$$\text{total current} = I'_{5\Omega} + I''_{5\Omega} + I'''_{5\Omega}$$

$$= 0 + 25A + 7A$$


$$I = 32A$$

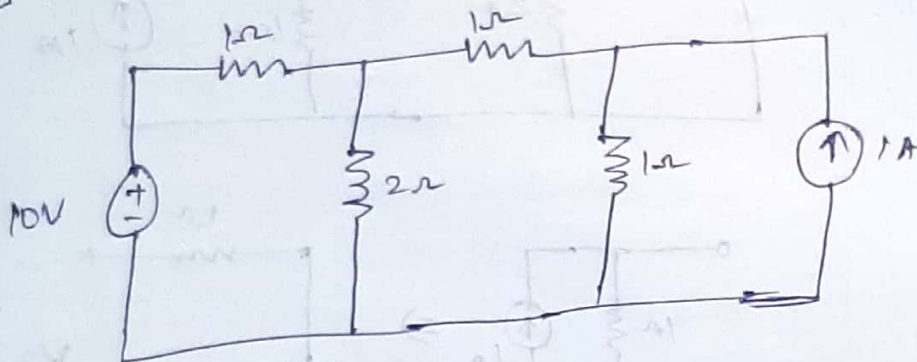③ Calculate the current through  $2\Omega$  resistor by using Superposition theorem.



Solution:

Step 1: Consider 10V,

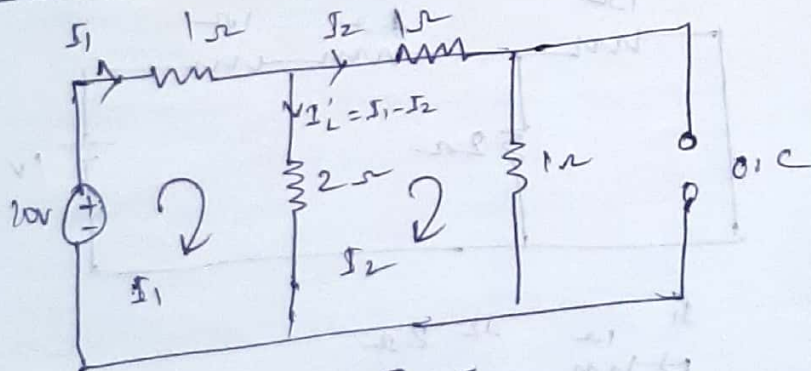

$$[R] [I] = [V]$$





$$\begin{bmatrix} 3 & -2 \\ -2 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$I_1 = 5A, I_2 = 2.5A$$

$$I_1' = I_1 - I_2 = 5 - 2.5$$

$$I_1' = 2.5A$$

Step: 2: Consider 1 A Source.

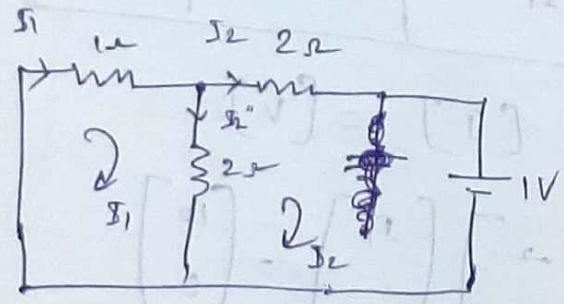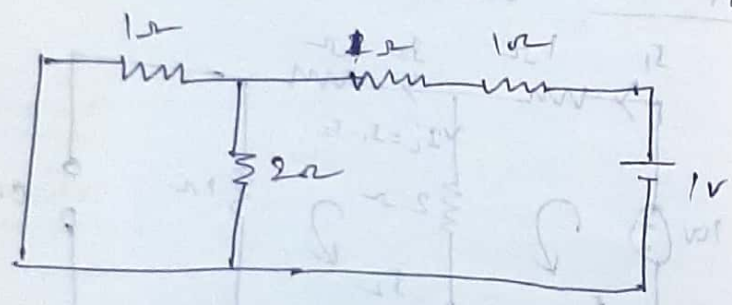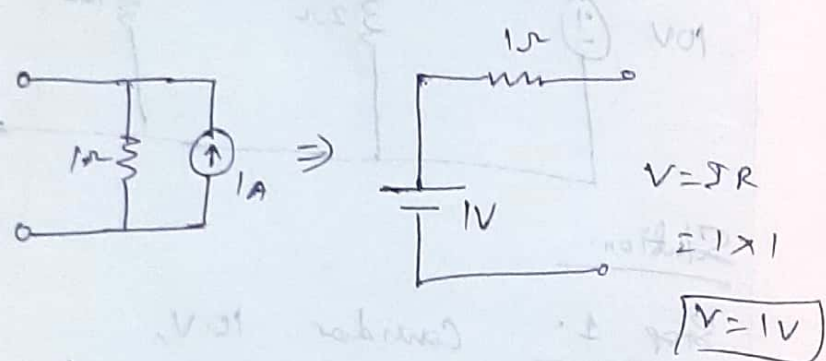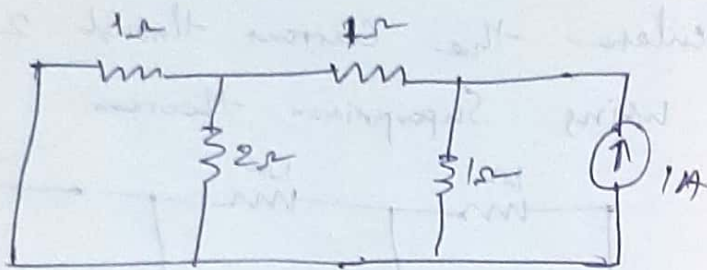



$$\begin{bmatrix} 3 & -2 \\ -2 & 4 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

$$J_1 = -0.25, \quad J_2 = -0.375$$

$$J_L'' = J_1 - J_2$$

$$= -0.25 - (-0.37) = -0.25 + 0.375$$

$$J_L'' = 0.125 \text{ A}$$

Step 3: Consider both sources.


$$J_L = J_L' + J_L''$$

$$= 2.5 + 0.125$$

$$J_L = 2.625 \text{ A}$$




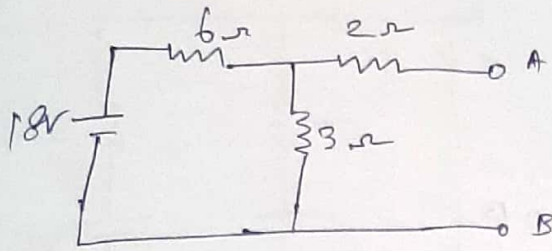② Draw the Norton's equivalent circuit across A & B. for the given circuit.



Solution:

Find  $V_{th}$ .

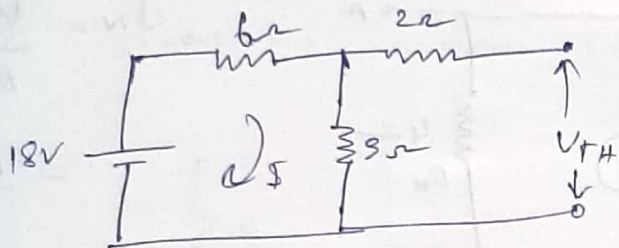


$$V_{AB} = I \times 3 = V_{th}$$

$$I = \frac{18}{6+3} = \frac{18}{9} = 2 \text{ A}$$

$$V_{th} = 2 \times 3 = 6 \text{ V}$$

$$V_{th} = 6 \text{ V}$$

Find  $R_{th}$

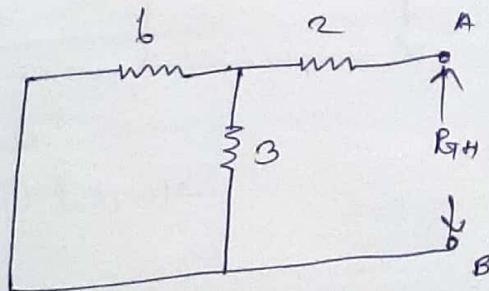

$$R_{th} = \frac{6 \times 3}{6+3} + 2$$


$$= \frac{18}{9} + 2$$

$$= 2 + 2$$


$$R_{th} = 4 \Omega$$



Draw thevenin's equivalent circuit.

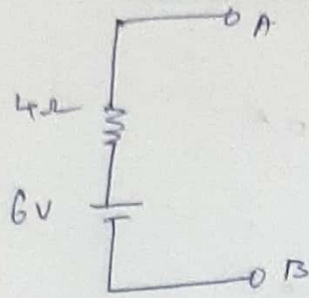

Norton's Equivalent circuit

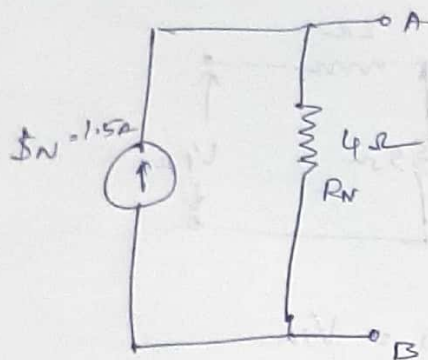

$$I_N = \frac{V_{TH}}{R_{TH}}$$

$$= \frac{6}{4} = 1.5A$$

$$I_N = 1.5A$$

$$R_N = R_{TH}$$

$$R_N = 4\Omega$$

$$V_d = 2V$$

